

Germanium Diode Crystal Radio

Chuck Honick Spencer Lyon

December 10, 2012

Some facts

- First used to receive Morse code signals
- Have since been to pick up vocal broadcasting signals
- No battery power; all energy is from radio waves received by antenna
- Reliable and cheap → popular
- No amplification = weak (quiet) signal

Some facts

- First used to receive Morse code signals
- Have since been to pick up vocal broadcasting signals
- No battery power; all energy is from radio waves received by antenna
- Reliable and cheap → popular
- No amplification = weak (quiet) signal

Some facts

- First used to receive Morse code signals
- Have since been to pick up vocal broadcasting signals
- No battery power; all energy is from radio waves received by antenna
- Reliable and cheap → popular
- No amplification = weak (quiet) signal

Some facts

- First used to receive Morse code signals
- Have since been to pick up vocal broadcasting signals
- No battery power; all energy is from radio waves received by antenna
- Reliable and cheap → popular
- No amplification = weak (quiet) signal

Some facts

- First used to receive Morse code signals
- Have since been to pick up vocal broadcasting signals
- No battery power; all energy is from radio waves received by antenna
- Reliable and cheap → popular
- No amplification = weak (quiet) signal

How it works

- 3 main parts
 - 1 Antenna
 - 2 Tuning circuit
 - 3 Semiconductor crystal detector
- Also, to hear the signal you need a speaker or earpiece

How it works

- 3 main parts
 - 1 Antenna
 - 2 Tuning circuit
 - 3 Semiconductor crystal detector
- Also, to hear the signal you need a speaker or earpiece

How it works

- 3 main parts
 - 1 Antenna
 - 2 Tuning circuit
 - 3 Semiconductor crystal detector
- Also, to hear the signal you need a speaker or earpiece

How it works

- 3 main parts
 - 1 Antenna
 - 2 Tuning circuit
 - 3 Semiconductor crystal detector
- Also, to hear the signal you need a speaker or earpiece

How it works

- 3 main parts
 - ① Antenna
 - ② Tuning circuit
 - ③ Semiconductor crystal detector
- Also, to hear the signal you need a speaker or earpiece

Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be $\frac{1}{4}$ of signal wavelength
 - common AM radio frequency (f) range is $(531 - 1611) \text{ kHz}$
 - wavelength: $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{f}$ or range $(186 - 358) \text{ m}$
 - ideal antenna length $l = \lambda/4 = (46 - 89) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be $\frac{1}{4}$ of signal wavelength
 - common AM radio frequency (f) range is $(531 - 1611)kHz$
 - wavelength: $\lambda = \frac{c}{f} = \frac{3 \times 10^8 m/sec}{fHz} \rightarrow \text{range } (186 - 564)m$
 - Ideal antenna length $l = \lambda/4 = (46 - 141)m$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be $\frac{1}{4}$ of signal wavelength
 - common AM radio frequency (f) range is (531 – 1611)kHz
 - wavelength: $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
 - Ideal antenna length $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be $\frac{1}{4}$ of signal wavelength
 - common AM radio frequency (f) range is (531 – 1611)kHz
 - wavelength: $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
 - Ideal antenna length $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be $\frac{1}{4}$ of signal wavelength
 - common AM radio frequency (f) range is (531 – 1611)kHz
 - wavelength: $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
 - Ideal antenna length $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be $\frac{1}{4}$ of signal wavelength
 - common AM radio frequency (f) range is (531 – 1611)kHz
 - wavelength: $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
 - Ideal antenna length $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be $\frac{1}{4}$ of signal wavelength
 - common AM radio frequency (f) range is (531 – 1611)kHz
 - wavelength: $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
 - Ideal antenna length $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

Our antenna

- We tried two different antennas
 - ① 25 ft (7.62 m) of aluminum single strand insulated wire
 - ② 72 ft (21.95 m) of copper single strand insulated wire
- Recall that optimal antenna length is between 46-141 m
- Copper wire did much better than the aluminum

Our antenna

- We tried two different antennas
 - ① 25 ft (7.62 m) of aluminum single strand insulated wire
 - ② 72 ft (21.95 m) of copper single strand insulated wire
- Recall that optimal antenna length is between 46-141 m
- Copper wire did much better than the aluminum

Our antenna

- We tried two different antennas
 - ① 25 ft (7.62 m) of aluminum single strand insulated wire
 - ② 72 ft (21.95 m) of copper single strand insulated wire
- Recall that optimal antenna length is between 46-141 m
- Copper wire did much better than the aluminum

Our antenna

- We tried two different antennas
 - ① 25 ft (7.62 m) of aluminum single strand insulated wire
 - ② 72 ft (21.95 m) of copper single strand insulated wire
- Recall that optimal antenna length is between 46-141 m
- Copper wire did much better than the aluminum

Our antenna

- We tried two different antennas
 - ① 25 ft (7.62 m) of aluminum single strand insulated wire
 - ② 72 ft (21.95 m) of copper single strand insulated wire
- Recall that optimal antenna length is between 46-141 m
- Copper wire did much better than the aluminum

Tuning circuit theory

- Consists of a solenoid (L) and a capacitor (C)
- Works a lot like a tuning fork (resonance)
- Current flows between the capacitor and the solenoid
- The received signal frequency matches the resonant frequency of the LC circuit ($f = \frac{1}{2\pi\sqrt{LC}}$)
- Different "loops" on the solenoid allow the user to change inductance ($L = \frac{\mu N^2 A}{l}$) and therefore change resonant frequency

Tuning circuit theory

- Consists of a solenoid (L) and a capacitor (C)
- Works a lot like a tuning fork (resonance)
- Current flows between the capacitor and the solenoid
- The received signal frequency matches the resonant frequency of the LC circuit ($f = \frac{1}{2\pi\sqrt{LC}}$)
- Different "loops" on the solenoid allow the user to change inductance ($L = \frac{\mu N^2 A}{l}$) and therefore change resonant frequency

Tuning circuit theory

- Consists of a solenoid (L) and a capacitor (C)
- Works a lot like a tuning fork (resonance)
- Current flows between the capacitor and the solenoid
- The received signal frequency matches the resonant frequency of the LC circuit ($f = \frac{1}{2\pi\sqrt{LC}}$)
- Different "loops" on the solenoid allow the user to change inductance ($L = \frac{\mu N^2 A}{l}$) and therefore change resonant frequency

Tuning circuit theory


- Consists of a solenoid (L) and a capacitor (C)
- Works a lot like a tuning fork (resonance)
- Current flows between the capacitor and the solenoid
- The received signal frequency matches the resonant frequency of the LC circuit ($f = \frac{1}{2\pi\sqrt{LC}}$)
- Different "loops" on the solenoid allow the user to change inductance ($L = \frac{\mu N^2 A}{l}$) and therefore change resonant frequency

Tuning circuit theory

- Consists of a solenoid (L) and a capacitor (C)
- Works a lot like a tuning fork (resonance)
- Current flows between the capacitor and the solenoid
- The received signal frequency matches the resonant frequency of the LC circuit ($f = \frac{1}{2\pi\sqrt{LC}}$)
- Different "loops" on the solenoid allow the user to change inductance ($L = \frac{\mu N^2 A}{l}$) and therefore change resonant frequency

Our tuning circuit

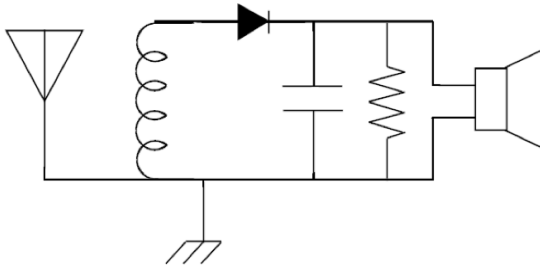- To build the tuning circuit, we followed this circuit diagram



- Our solenoid has 60 turns ($N = 60$)
- Capacitor value: $0.001 \mu F$
- Resistor value: $82 k\Omega$

Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

Audio output

- We initially tried headphones, but they didn't work
 - Input impedance was too low
 - No signal or sound amplification
- We then used externally powered speakers
 - Much better because impedance was very high
 - External power amplified the audio signal

Audio output

- We initially tried headphones, but they didn't work
 - Input impedance was too low
 - No signal or sound amplification
- We then used externally powered speakers
 - Much better because impedance was very high
 - External power amplified the weak signal

Audio output

- We initially tried headphones, but they didn't work
 - Input impedance was too low
 - No signal or sound amplification
- We then used externally powered speakers
 - Much better because impedance was very high
 - External power amplified the audio signal

Audio output

- We initially tried headphones, but they didn't work
 - Input impedance was too low
 - No signal or sound amplification
- We then used externally powered speakers
 - Much better because impedance was very high
 - External power amplified the sound signal


Audio output

- We initially tried headphones, but they didn't work
 - Input impedance was too low
 - No signal or sound amplification
- We then used externally powered speakers
 - Much better because impedance was very high
 - External power amplified the sound signal

Audio output

- We initially tried headphones, but they didn't work
 - Input impedance was too low
 - No signal or sound amplification
- We then used externally powered speakers
 - Much better because impedance was very high
 - External power amplified the sound signal

The Final Product

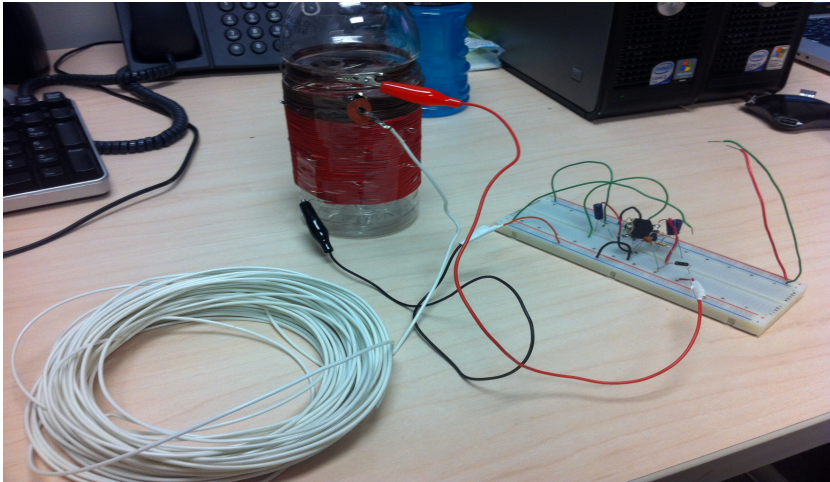

Demo

- Tune in to 1280 The Zone!

Interpretation

- There are many ways we could improve our radio
 - Tune the antenna with capacitor which increases the signal/noise ratio
 - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
 - Include a signal (or audio) amplifier to make signal to the audio device stronger
 - Build a larger solenoid and/or use longer antenna

Interpretation

- There are many ways we could improve our radio
 - Tune the antenna with capacitor which increases the signal/noise ratio
 - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
 - Include a signal (or audio) amplifier to make signal to the audio device stronger
 - Build a larger solenoid and/or use longer antenna

Interpretation

- There are many ways we could improve our radio
 - Tune the antenna with capacitor which increases the signal/noise ratio
 - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
 - Include a signal (or audio) amplifier to make signal to the audio device stronger
 - Build a larger solenoid and/or use longer antenna

Interpretation

- There are many ways we could improve our radio
 - Tune the antenna with capacitor which increases the signal/noise ratio
 - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
 - Include a signal (or audio) amplifier to make signal to the audio device stronger
 - Build a larger solenoid and/or use longer antenna

Interpretation

- There are many ways we could improve our radio
 - Tune the antenna with capacitor which increases the signal/noise ratio
 - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
 - Include a signal (or audio) amplifier to make signal to the audio device stronger
 - Build a larger solenoid and/or use longer antenna