

# Germanium Diode Crystal Radio

Chuck Honick    Spencer Lyon

December 11, 2012

## Some facts

- First used to receive Morse code signals
- Have since been to pick up vocal broadcasting signals
- No battery power; all energy is from radio waves received by antenna
- Reliable and cheap → popular
- No amplification = weak (quiet) signal

# How it works

- 3 main parts
  - ① Antenna
  - ② Tuning circuit
  - ③ Semiconductor crystal detector
- Also, to hear the signal you need a speaker or earpiece

# Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be  $\frac{1}{4}$  of signal wavelength
  - common AM radio frequency ( $f$ ) range is  $(531 - 1611) \text{ kHz}$
  - wavelength:  $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{f} \Rightarrow \text{range } (188 - 358) \text{ m}$
  - ideal antenna length  $l = \lambda/4 = (47 - 89) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

# Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be  $\frac{1}{4}$  of signal wavelength
  - common AM radio frequency ( $f$ ) range is  $(531 - 1611)kHz$
  - wavelength:  $\lambda = \frac{c}{f} = \frac{3 \times 10^8 m/sec}{fHz} \rightarrow \text{range } (186 - 564)m$
  - Ideal antenna length  $l = \lambda/4 = (46 - 141)m$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

# Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be  $\frac{1}{4}$  of signal wavelength
  - common AM radio frequency ( $f$ ) range is (531 – 1611)kHz
  - wavelength:  $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
  - Ideal antenna length  $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

# Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be  $\frac{1}{4}$  of signal wavelength
  - common AM radio frequency ( $f$ ) range is (531 – 1611)kHz
  - wavelength:  $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range (186 – 564)m}$
  - Ideal antenna length  $l = \lambda/4 = (46 – 141)\text{m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

# Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be  $\frac{1}{4}$  of signal wavelength
  - common AM radio frequency ( $f$ ) range is (531 – 1611)kHz
  - wavelength:  $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
  - Ideal antenna length  $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)



# Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be  $\frac{1}{4}$  of signal wavelength
  - common AM radio frequency ( $f$ ) range is (531 – 1611)kHz
  - wavelength:  $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{fHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
  - Ideal antenna length  $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

# Antenna Theory

- Converts energy in electromagnetic radio waves to AC current
- For best performance, antenna length should be  $\frac{1}{4}$  of signal wavelength
  - common AM radio frequency ( $f$ ) range is (531 – 1611)kHz
  - wavelength:  $\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/sec}}{\text{kHz}} \rightarrow \text{range } (186 - 564) \text{ m}$
  - Ideal antenna length  $l = \lambda/4 = (46 - 141) \text{ m}$
- Antenna is only "power source" in the circuit
- Larger antenna results in more power (louder signal)

# Our antenna

- We tried two different antennas
  - ① 25 ft (7.62 m) of aluminum single strand insulated wire
  - ② 72 ft (21.95 m) of copper single strand insulated wire
- Recall that optimal antenna length is between 46-141 m
- Copper wire did much better than the aluminum

# Tuning circuit theory

- Consists of an inductor (L) and a capacitor (C)
- Current flows between the capacitor and the solenoid
- Works a lot like a tuning fork (resonance)
- The received signal frequency matches the resonant frequency of the LC circuit ( $f = \frac{1}{2\pi\sqrt{LC}}$ )
- Different "loops" on the solenoid allow the user to change inductance ( $L = \frac{\mu N^2 A}{l}$ ) and therefore change resonant frequency

# Tuning circuit theory

- Consists of an inductor (L) and a capacitor (C)
- Current flows between the capacitor and the solenoid
- Works a lot like a tuning fork (resonance)
- The received signal frequency matches the resonant frequency of the LC circuit ( $f = \frac{1}{2\pi\sqrt{LC}}$ )
- Different "loops" on the solenoid allow the user to change inductance ( $L = \frac{\mu N^2 A}{l}$ ) and therefore change resonant frequency

# Tuning circuit theory

- Consists of an inductor (L) and a capacitor (C)
- Current flows between the capacitor and the solenoid
- Works a lot like a tuning fork (resonance)
- The received signal frequency matches the resonant frequency of the LC circuit ( $f = \frac{1}{2\pi\sqrt{LC}}$ )
- Different "loops" on the solenoid allow the user to change inductance ( $L = \frac{\mu N^2 A}{l}$ ) and therefore change resonant frequency

# Tuning circuit theory

- Consists of an inductor (L) and a capacitor (C)
- Current flows between the capacitor and the solenoid
- Works a lot like a tuning fork (resonance)
- The received signal frequency matches the resonant frequency of the LC circuit ( $f = \frac{1}{2\pi\sqrt{LC}}$ )
- Different "loops" on the solenoid allow the user to change inductance ( $L = \frac{\mu N^2 A}{l}$ ) and therefore change resonant frequency


# Tuning circuit theory

- Consists of an inductor (L) and a capacitor (C)
- Current flows between the capacitor and the solenoid
- Works a lot like a tuning fork (resonance)
- The received signal frequency matches the resonant frequency of the LC circuit ( $f = \frac{1}{2\pi\sqrt{LC}}$ )
- Different "loops" on the solenoid allow the user to change inductance ( $L = \frac{\mu N^2 A}{l}$ ) and therefore change resonant frequency


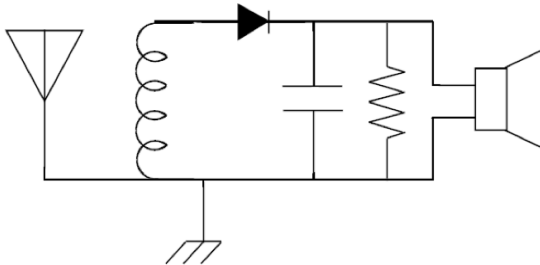
## Our tuning circuit

- To build the tuning circuit, we followed this circuit diagram



- Our solenoid has 60 turns ( $N = 60$ )
- Capacitor value:  $0.001 \mu F$
- Resistor value:  $82 k\Omega$

# Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency components
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

# Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency components
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

# Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency components
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

# Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency components
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)


# Semiconductor crystal detector

- Rectifies the AM frequency leaving only positive frequency components
- This frequency is then filtered with a resistor and capacitor and fed to audio device
- Old crystal radios used Galena (lead sulfide), but that isn't the most efficient
- Germanium diodes are optimal because a low forward voltage drop makes them more sensitive
- We used a NTE109 Germanium diode (fast-switching)

# Audio output

- We initially tried headphones, but they didn't work
  - Input impedance was too low
  - No signal or sound amplification
- We then used externally powered speakers
  - Much better because impedance was very high
  - External power amplified the sound signal

# The Final Product

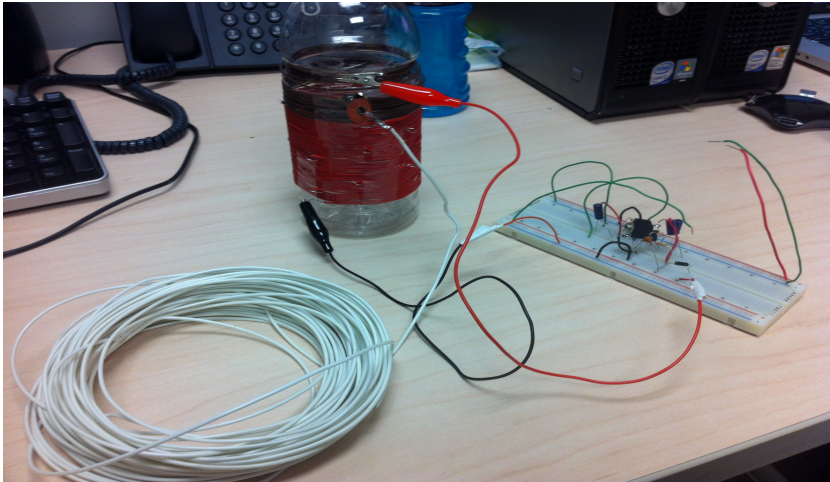



# Demo

- Tune in to 1280 The Zone!

# Interpretation

- There are many ways we could improve our radio
  - Tune the antenna with capacitor which increases the signal/noise ratio
  - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
  - Include a signal (or audio) amplifier to make signal to the audio device stronger
  - Build a larger solenoid and/or use longer antenna

# Interpretation

- There are many ways we could improve our radio
  - Tune the antenna with capacitor which increases the signal/noise ratio
  - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
  - Include a signal (or audio) amplifier to make signal to the audio device stronger
  - Build a larger solenoid and/or use longer antenna

# Interpretation

- There are many ways we could improve our radio
  - Tune the antenna with capacitor which increases the signal/noise ratio
  - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
  - Include a signal (or audio) amplifier to make signal to the audio device stronger
  - Build a larger solenoid and/or use longer antenna

# Interpretation

- There are many ways we could improve our radio
  - Tune the antenna with capacitor which increases the signal/noise ratio
  - We have single capacitor for filter, using a variable capacitor would allow us to pick up different frequencies
  - Include a signal (or audio) amplifier to make signal to the audio device stronger
  - Build a larger solenoid and/or use longer antenna